

II B. Tech II Semester Regular Examinations, August/September - 2021

DIGITAL ELECTRONICS

(Electrical and Electronics Engineering)


Time: 3 hours

Max. Marks: 75


Answer any **FIVE** Questions each Question from each unit

All Questions carry **Equal** Marks

- ~~~~~
- 1 a) Given the two binary numbers $X = 1010101$ and $Y = 1001011$, perform the subtraction $X-Y$ using 1's and 2's complements. [8M]
 b) Given the Boolean function: $F=xy+x'y'+y'z$ (i) Implement it with only OR and NOT gates. (ii) Implement it with only AND and NOT gates. [7M]
- Or
- 2 a) Convert $(347)_{10}$ into $()_2$, $()_8$, $()_5$, $()_{16}$, and $()_{BCD}$. [8M]
 b) Realize 2 input X-OR gate and 2 input X-NOR gates using NAND gates only. [7M]
- 3 a) Simplify the following Boolean expressions by manipulation of Boolean algebra. [8M]
 1. $F(x,y,z)=xy+xyz+xyz'+x'yz$
 2. $F(A,B,C,D)=A'C(A'BD)'+A'BC'D'+AB'C$
 b) Simplify the following function using Karnaugh maps $f(x, y, w, z) = \sum m (0, 1, 2, 3, 7, 8, 10) + \sum d (5, 6, 11, 15)$, where d represents the don't-care condition. [7M]
- Or
- 4 a) Define duality principle and explain it with the help of example. Find the complements of the functions $F1 = x'yz' + x'y'z$ and $F2 = x(y'z'+yz)$ by taking their duals and complementing each literal. [7M]
 b) What is the significance of tabular minimization? Simplify the function $F(A,B,C,D,E)=\sum m(0,2,4,6,9,11,13,15)$ using tabular minimization. [8M]
- 5 a) Design Half adder and full adder using gates. [8M]
 b) Implement the following function with a multiplexer: $F(A, B, C) = \sum m(0, 2, 4, 7)$. [7M]
- Or
- 6 a) Obtain an 8×1 multiplexer with a dual 4-line to 1-line multiplexers having separate enable inputs but common selection lines. [7M]
 b) design a BCD-to-Seven segment decoder. [8M]
- 7 a) Explain clocked RS flip flop with the help of logic diagram and truth table. [7M]
 b) Design a Mod 7 binary counter. Draw its state diagram and circuit. [8M]
- Or
- 8 a) Explain clocked D flip flop with NAND gates only? Define the working of D flip flop with truth table. [7M]
 b) Design 3-bit binary counter using T flip-flop. [8M]

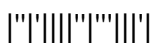

 - 9 a) Distinguish between Mealy and Moore Machines. [7M]
 b) Give the state table for the given state diagram. Also give the state assignment [8M]



Or

- 10 a) What is meant by State Reduction? Explain Partitioning Method of State Reduction. [7M]
 b) For the given Moore machine transition table Convert into Mealy machine. [8M]

Present State	Next State		Output
	a = 0	a = 1	
q ⁰	q ³	q ¹	1
q ¹	q ⁰	q ³	0
q ²	q ²	q ²	0
q ³	q ¹	q ⁰	1

