

**III B. Tech I Semester Supplementary Examinations, June/July-2022**  
**ELECTRONIC MEASUREMENTS & INSTRUMENTATION**

(Electronics and Communication Engineering)

Time: 3 hours

Max. Marks: 75

Answer any **FIVE** Questions **ONE** Question from **Each unit**

All Questions Carry Equal Marks

\*\*\*\*\*

**UNIT-I**

1. a) Explain in detail the different types of errors in measuring instruments. [8M]  
b) Explain with neat circuit diagram the working of any one type of digital voltmeter. [7M]

**(OR)**

2. a) A basic D'Arsonval movement with a full deflection of 50  $\mu$ A and internal resistance of 500  $\Omega$  is used as voltmeter. Formulate the necessary equation and calculate the value of multiplier resistance needed to measure a voltage range of 0-10 V. [8M]  
b) How is multi-meter used to measure different parameters? Explain. [7M]

**UNIT-II**

3. a) Draw the block diagram of an audio spectrum analyzer. Explain its operation. [8M]  
b) Define a Wave Analyzer and list its types. [7M]

**(OR)**

4. a) With neat sketch explain the working principle of function generator. [8M]  
b) What are the different Types of Harmonic Distortion? Define Total Harmonic Distortion (THD). [7M]

**UNIT-III**

5. a) Explain the internal structure of CRT and describe the principle of electrostatic focusing. [8M]  
b) Compare analog storage oscilloscope and digital storage oscilloscope. [7M]

**(OR)**

6. a) Explain the modes of operation of digital storage oscilloscope. [8M]  
b) Describe the different types of sweeps used in CRO. [7M]



**UNIT-IV**

7. a) Describe the circuit of Kelvin double bridge used for measurement of low resistance. Derive the conditions for balance. [8M]
- b) An AC bridge has the following constants: [7M]  
Arm AB- Capacitor of  $0.5 \mu\text{F}$  in parallel with  $1 \text{ k}\Omega$  resistance.  
Arm AD- resistance of  $2 \text{ k}\Omega$ .  
Arm DC-Capacitor of  $0.5 \mu\text{F}$ .  
Arm CD-Unknown  $C_x$  and  $R_x$  in series, frequency  $1 \text{ kHz}$ .  
Determine the unknown capacitance and dissipation factor.

**(OR)**

8. a) Explain the theory and working principle of Whetstone's Bridge. Derive the relation for finding unknown resistance. [8M]
- b) With neat sketch explain the basic block diagram of the counter in time interval mode for measuring time interval. [7M]

**UNIT-V**

9. a) How the transducers are classified on the basis of principle of operation? Discuss. [8M]
- b) With neat diagram explain potentiometer resistance transducer. List advantages and disadvantages. [7M]

**(OR)**

10. a) With a neat sketch explain LVDT for velocity measurement. [8M]
- b) Explain how to measure temperature? [7M]

\*\*\*\*\*

