

II B. Tech II Semester Regular/Supplementary Examinations, November - 2020
PULSE AND DIGITAL CIRCUITS

(Com to ECE, EIE, ECC)

Time: 3 hours

Max. Marks: 70

- Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)
 2. Answer **ALL** the question in **Part-A**
 3. Answer any **FOUR** Questions from **Part-B**
- ~~~~~

PART -A

1. a) Define the terms rise time t_r , fall time t_f and tilt in a practical pulse waveform (2M)
- b) Draw the transfer characteristics of clamper (2M)
- c) How diode act as a switch? (3M)
- d) Mention the applications of AstableMultivibrator (2M)
- e) Write short note on Negative Resistance Switches (3M)
- f) Compare the different logic families (2M)

PART -B

2. a) Obtain the response of an RC low-pass circuit to a square wave input for long, medium and short time constants. (7M)
- b) Show that an RC low-pass circuit can be used as an Integrator. (7M)
3. a) Design a two level clipper for bias voltages $V_1 = 5V$ and $V_2 = -5V$. Use practical diodes. (7M)
- b) Explain the effect of diode characteristics on clamping voltage. (7M)
4. a) Explain the saturation parameters of transistor and their variation with temperature (7M)
- b) Explain the operation of emitter coupled Bistablemultivibrator (7M)
5. a) A collector coupled monostablemultivibrator using n-p-n silicon transistors has the following parameters: $V_{CC} = 12V$, $V_{BB} = 3V$, $R_C = 2k$, $R_1 = R_2 = R = 20k$, $h_{FE} = 30$, $r_{bb} = 200\Omega$, and $C = 1000$ PF. Neglect I_{CBO} .
 (i) Calculate and plot to scale the wave shapes at each base and collector.
 (ii) Find the width of the output pulse.
- b) Explain the application of AstableMultivibrator as a voltage to frequency converter (7M)
6. a) Draw and explain exponential sweep circuit (7M)
- b) Draw the circuit diagram of Bootstrap time base generator and explain the operation with the help of a waveforms. (7M)
7. a) Explain with a neat circuit diagram the operation of ECL OR/NOR gate (7M)
- b) Compare unidirectional and bidirectional sampling gates. (7M)